

ECC Summer School 2004


Hardware Implementation of ECC

Jan Pelzl

Communications Security Group

Ruhr-Universität Bochum

<http://www.crypto.rub.de>

 

Overview

● Overview

Introduction


Hardware Design

Hardware for $GF(2^n)$

Hardware for $GF(p)$

Practical Performance

 1. Introduction
 - Why Hardware Acceleration?
 - What is Hardware?
2. Hardware Design
 - Design Process
 - Example
3. Hardware for $GF(2^n)$
 - Number Representations
 - Addition, Subtraction
 - Squaring
 - Multiplication
 - Reduction
4. Hardware for $GF(p)$
 - Number Representations
 - Addition, Subtraction
 - Squaring, Multiplication
 - Reduction
5. Practical Performance
 - Examples



Why Hardware Acceleration?

- Overview

- Introduction

- Why Hardware Acceleration?

- What is Hardware?

- Tradeoff ASIC vs. FPGA

- Hardware Design

- Hardware for $GF(2^n)$


- Hardware for $GF(p)$

- Practical Performance

Hardware (HW) acceleration required if conventional processors too slow.

⇒ two scenarios:

 1. **High end server** with many (thousands) PK operations per second
 - Let HW do computational expensive PK operations
 - Example: SSL - Server
2. **Embedded device** with low power CPU (cheap)
 - HW extension to enable for PK cryptography
 - Examples: Mobiles, low-end PDA, smart cards



What is Hardware?

- Overview

- Introduction

- Why Hardware Acceleration?

- What is Hardware?

- Tradeoff ASIC vs. FPGA

- Hardware Design


- Hardware for $GF(2^n)$

- Hardware for $GF(p)$

- Practical Performance

Electronic circuit designed mainly for a **single purpose** (aka special purpose hardware).

 - Application Specific Integrated Circuit (**ASIC**)
(=chip for one special application)
- Field Programmable Gate Array (**FPGA**)
(=reprogrammable circuit, additional logic)



Tradeoff ASIC vs. FPGA

● Overview

Introduction

- Why Hardware Acceleration?
- What is Hardware?
- Tradeoff ASIC vs. FPGA

Hardware Design

Hardware for $GF(2^n)$

Hardware for $GF(p)$

Practical Performance

time to market

cost (high quantity)

cost (low quantity)

integration

development costs

 


Figure 1: Comparison ASIC vs. FPGA



Design Process

● Overview

Introduction

Hardware Design

● Design Process

● Design Process (2)

● Example


Hardware for $GF(2^n)$


Hardware for $GF(p)$

Practical Performance

Objective: Project structure and interaction of different functional units onto specific hardware.

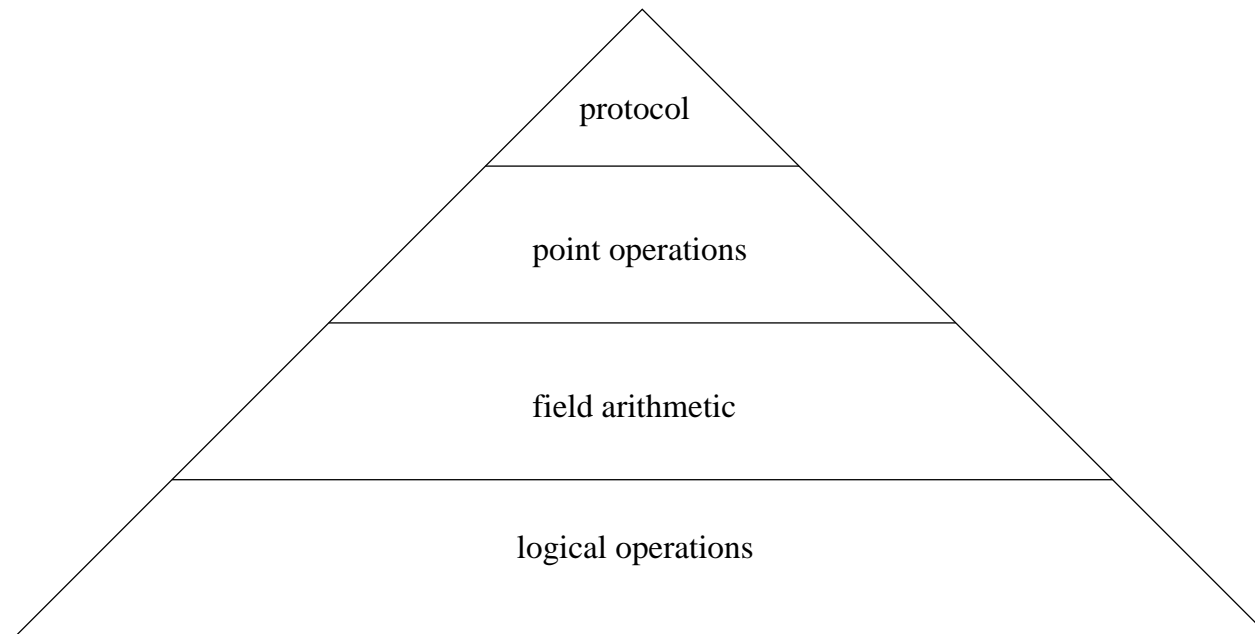E.g., Functionality of an elliptic curve cryptosystem:



 

Design Process (2)

● Overview

Introduction

Hardware Design

● Design Process

● Design Process (2)


● Example


Hardware for $GF(2^n)$

Hardware for $GF(p)$

Practical Performance

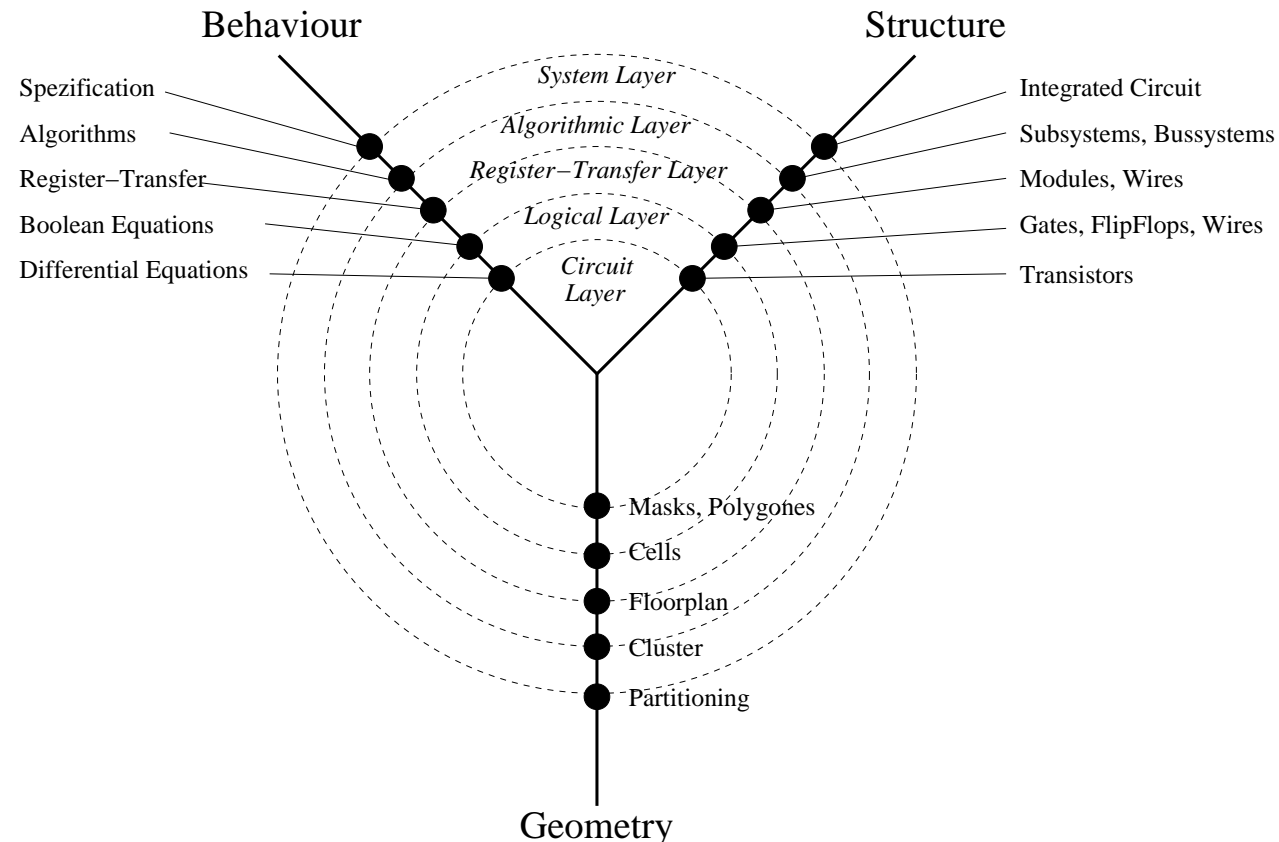Different design methods available, e.g., use Gajski Y-Diagram to specify 3 approaches to the hardware:



 

Example

● Overview

Introduction

Hardware Design

● Design Process

● Design Process (2)


● Example


Hardware for $GF(2^n)$

Hardware for $GF(p)$

Practical Performance

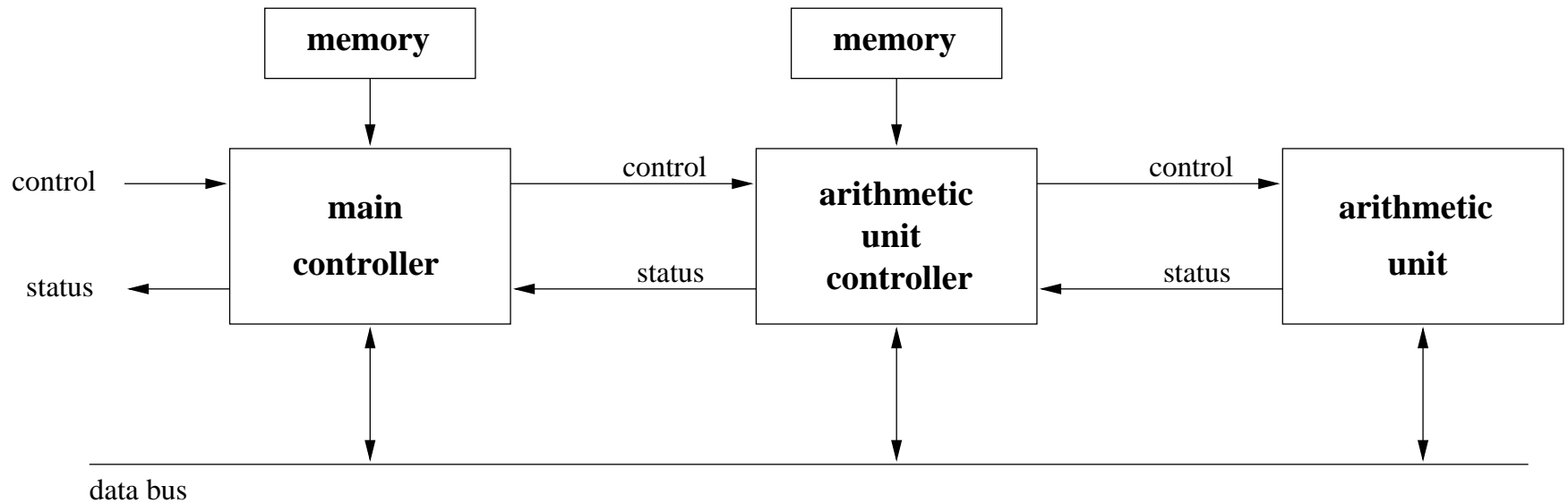Processor Architecture for ECC (subsystems) [OP00]:



 

Number Representation

● Overview

Introduction

Hardware Design

Hardware for $GF(2^n)$

● Number Representation

● Addition, Subtraction

● Squaring

● Multiplication

● Multiplication (2)

● Multiplication (3)

● Reduction

Hardware for $GF(p)$

Practical Performance

Most popular basis for numbers in $GF(2^n)$:


■ Polynomial basis:

- ◆ specified by an irreducible polynomial $f(z)$ modulo 2 (field polynomial)
- ◆ bit string $(a_{n-1}a_{n-2}\dots a_1a_0)$ represents polynomial $a_{n-1}z^{n-1} + \dots + a_1z + a_0$
- ◆ field arithmetic is implemented as polynomial arithmetic modulo $f(z)$

■ Normal basis:

- ◆ specified by an element θ
- ◆ bit string $(a_{n-1}a_{n-2}\dots a_1a_0)$ represents element $a_0\theta + a_1\theta^2 + a_2\theta^{2^2} + \dots + a_{n-1}\theta^{2^{n-1}}$
- ◆ for special classes of normal basis (**Type T low-complexity normal basis**), efficient implementations possible

 In HW, polynomial basis advantageous. (focus here)



Addition, Subtraction

● Overview

Introduction

Hardware Design

Hardware for $GF(2^n)$

● Number Representation

● Addition, Subtraction

● Squaring

● Multiplication

● Multiplication (2)

● Multiplication (3)

● Reduction


Hardware for $GF(p)$


Practical Performance

In Hardware,

- addition and subtraction over $GF(2^n)$ by **bitwise XOR**
- variables of **arbitrary bit length** can be processed simultaneously

$$c = a \pm b = a \oplus b$$

 

 

Squaring

● Overview

Introduction

Hardware Design

Hardware for $GF(2^n)$

- Number Representation
- Addition, Subtraction

● Squaring


- Multiplication
- Multiplication (2)
- Multiplication (3)
- Reduction


Hardware for $GF(p)$

Practical Performance

No complicated logic required, **only routing** of input bits to correct output positions:

$$c = a^2$$

 

 

Multiplication

● Overview

Introduction

Hardware Design

Hardware for $GF(2^n)$

- Number Representation
- Addition, Subtraction
- Squaring

● Multiplication

- Multiplication (2)
- Multiplication (3)
- Reduction

Hardware for $GF(p)$


Practical Performance

Array type multiplication:

- n multiplicand bits are processed in parallel
- multiplier bits are processed one bit each step
- polynomial multiplication and reduction are interleaved each step

The array type multiplication can be performed in two major ways:

 - Least Significant Bit first (**LSB** first)
- Most Significant Bit first (**MSB** first)



Multiplication (2)

● Overview

Introduction

Hardware Design

Hardware for $GF(2^n)$

● Number Representation

● Addition, Subtraction

● Squaring

● Multiplication

● Multiplication (2)

● Multiplication (3)

● Reduction

Hardware for $GF(p)$

Practical Performance

Let $A = \sum_{j=0}^{n-1} a_j z^j$, $B = \sum_{j=0}^{n-1} b_j z^j$, and $C = \sum_{j=0}^{n-1} c_j z^j$ the product of A and B .

LSB first multiplication:

$$\begin{aligned} C &= AB \bmod f(z) \\ &= b_0 A + b_1 (A \cdot z \bmod f(z)) \\ &\quad + b_2 (A \cdot z^2 \bmod f(z)) \\ &\quad + \dots + b_{n-1} (A \cdot z^{n-1} \bmod f(z)) \end{aligned}$$

MSB first multiplication:

$$\begin{aligned} C &= AB \bmod f(z) \\ &= (\dots (A \cdot b_{n-1} \cdot z \bmod f(z) \\ &\quad + A \cdot b_{n-2}) \cdot z \bmod f(z) \\ &\quad + \dots + A \cdot b_1) \cdot z \bmod f(z) + A \cdot b_0 \end{aligned}$$



Multiplication (3)

- Overview

- Introduction

- Hardware Design

- Hardware for $GF(2^n)$

- Number Representation
- Addition, Subtraction
- Squaring
- Multiplication
- Multiplication (2)
- Multiplication (3)
- Reduction


- Hardware for $GF(p)$

- Practical Performance

Digit Serial Multiplier (DSM):

- n multiplicand bits are processed in parallel
- D bits of multiplier are processed simultaneously each step
→ total number of steps: $\lceil n/D \rceil$
- polynomial multiplication and reduction are interleaved each step
- Most Significant Digit first (MSD fist) multiplier
- Least Significant Digit first (LSD fist) multiplier

 (For more details on $GF(2^n)$ multiplier in HW, refer to [SP98].)



Reduction

● Overview

Introduction

Hardware Design

Hardware for $GF(2^n)$


- Number Representation
- Addition, Subtraction
- Squaring
- Multiplication
- Multiplication (2)
- Multiplication (3)

● Reduction

Hardware for $GF(p)$

Practical Performance

 - In case of addition/ subtraction: simply add $f(z)$ to intermediate results if larger than $f(z)$.
→ can hardwire reduction polynomial
- In case of squaring by table lookup: shift and add $f(z)$ to eliminate all bit positions with '1'.
→ can hardwire reduction polynomial multiple times
- interleaved multiplication does not need additional reduction



Number Representation

● Overview

Introduction

Hardware Design

Hardware for $GF(2^n)$

Hardware for $GF(p)$

● Number Representation


- Addition
- Addition (2)
- Addition (3)
- Addition (4)
- Addition (5)
- Subtraction
- Multiplication
- Multiplication (2)
- Multiplication (3)
- Multiplication (4)
- Squaring
- Reduction

Practical Performance

Can express $a \in GF(p)$ in different ways:

- **binary form**: $a = (a_{n-1} \dots a_1 a_0)_2 = a_{n-1}2^{n-1} + \dots + a_12 + a_0$
- **redundant bit representation** (e.g., for carry save adders)
→ uses more bits than necessary to represent number
- **2's complement** for negative numbers:
 - ◆ Positive 2's complement numbers are represented as the simple binary.
 - ◆ Negative 2's complement numbers are represented as the binary number that when added to a positive number of the same magnitude equals zero.

integer		2's complement
signed	unsigned	
5	5	0000 0101
-5	251	1111 1011

 

Addition

● Overview

Introduction

Hardware Design

Hardware for $GF(2^n)$

Hardware for $GF(p)$

● Number Representation

● Addition

● Addition (2)

● Addition (3)

● Addition (4)

● Addition (5)

● Subtraction

● Multiplication

● Multiplication (2)

● Multiplication (3)


● Multiplication (4)

● Squaring


● Reduction

Practical Performance

 Simple adder for two input bits (**half-adder**):




A_i	B_i	S_i	C_{i+1}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

Addition (2)

 Simple adder for three input bits (**full-adder**):



A_i	B_i	C_i	S_i	C_{i+1}
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

● Overview

Introduction

Hardware Design

Hardware for $GF(2^n)$

Hardware for $GF(p)$

● Number Representation

● Addition

● Addition (2)

● Addition (3)

● Addition (4)

● Addition (5)

● Subtraction

● Multiplication

● Multiplication (2)


● Multiplication (3)

● Multiplication (4)

● Squaring

● Reduction

Practical Performance

 

Addition (3)

● Overview

Introduction

Hardware Design


Hardware for $GF(2^n)$


Hardware for $GF(p)$

- Number Representation
- Addition
- Addition (2)
- Addition (3)
- Addition (4)
- Addition (5)
- Subtraction
- Multiplication
- Multiplication (2)
- Multiplication (3)
- Multiplication (4)
- Squaring
- Reduction

Practical Performance

 Carry Propagate Adder (CPA): Latency $O(n)$



 

Addition (4)

● Overview

Introduction

Hardware Design


Hardware for $GF(2^n)$


Hardware for $GF(p)$

- Number Representation
- Addition
- Addition (2)
- Addition (3)
- Addition (4)
- Addition (5)
- Subtraction
- Multiplication
- Multiplication (2)
- Multiplication (3)
- Multiplication (4)
- Squaring
- Reduction

Practical Performance

Carry Save Adder (CSA): Latency $O(1)$

 

 

Addition (5)

- Overview

- Introduction

- Hardware Design

- Hardware for $GF(2^n)$

- Hardware for $GF(p)$

- Number Representation

- Addition

- Addition (2)

- Addition (3)

- Addition (4)

- Addition (5)

- Subtraction

- Multiplication

- Multiplication (2)

- Multiplication (3)

- Multiplication (4)

- Squaring

- Reduction

- Practical Performance

Other methods for addition:

- **Bit Serial Adder**

→ compute one bit at a time with fulladder

- **Carry Completion Sensing Adder**

→ figures out when all carries are computed

- **Carry Look-Ahead Adder**

→ extra logic to compute carry bits in advance

- **Carry Delay Adder**

→ two level CSA used for efficient multiplication

(See [Ç. K. Koç96] for overview of addition operations in HW.)



Subtraction

- Overview

- Introduction

- Hardware Design

- Hardware for $GF(2^n)$

- Hardware for $GF(p)$

- Number Representation

- Addition

- Addition (2)

- Addition (3)

- Addition (4)

- Addition (5)

- Subtraction

- Multiplication

- Multiplication (2)

- Multiplication (3)

- Multiplication (4)

- Squaring

- Reduction

- Practical Performance


Implement subtraction with addition:

$$a - b = a + b'$$

where b' is $\bar{b} + 1$ and \bar{b} the bit wise complement of b .
The highest carry bit af the addition is ignored.

 Example: Let $a = 13_{10} = (1101)_2$ and $b = 6_{10} = (0110)_2$

$$\begin{aligned}\bar{b} &= (1001)_2 \\ b' &= \bar{b} + 1 = 1010 \\ \Rightarrow a - b &= a + b' \\ &= (1101)_2 + (1010)_2 \\ &= (0111)_2 = 7_{10}\end{aligned}$$



Multiplication

- Overview

- Introduction

- Hardware Design

- Hardware for $GF(2^n)$

- Hardware for $GF(p)$

- Number Representation

- Addition

- Addition (2)

- Addition (3)

- Addition (4)

- Addition (5)

- Subtraction

- Multiplication

- Multiplication (2)

- Multiplication (3)

- Multiplication (4)

- Squaring

- Reduction

- Practical Performance

Different methods for modular multiplication:

- **Schoolbook:**


- add intermediate results
- reduce in the end

- **Interleaved:**

- interleaved multiplication and reduction
- keeps intermediate results small

- **Montgomery:**

 - alternative residue number system (RNS)
- interleaved multiplication and reduction



Multiplication (2)

- Overview

- Introduction

- Hardware Design

- Hardware for $GF(2^n)$

- Hardware for $GF(p)$

- Number Representation
- Addition
- Addition (2)
- Addition (3)
- Addition (4)
- Addition (5)
- Subtraction
- Multiplication
- Multiplication (2)
- Multiplication (3)
- Multiplication (4)
- Squaring
- Reduction

- Practical Performance


Interleaved multiplication with **shift-add** multiplication algorithm:

Require: $A < 2^k, B < 2^k$, modulus n

Ensure: $P = A \cdot B$ such that $0 \leq P \leq 3n$

 - 1: $P := 0$
- 2: **for** $i = 0$ to $k - 1$ **do**
- 3: $P := 2P + A \cdot B_{k-1-i}$
- 4: $P := P \bmod n$
- 5: **end for**
- 6: return P

Remark: Since $0 \leq P \leq 3n$ at most 2 subtractions of n are required in the end.



Multiplication (3)

● Overview

Introduction

Hardware Design

Hardware for $GF(2^n)$

Hardware for $GF(p)$

- Number Representation
- Addition
- Addition (2)
- Addition (3)
- Addition (4)
- Addition (5)
- Subtraction
- Multiplication
- Multiplication (2)
- Multiplication (3)
- Multiplication (4)
- Squaring
- Reduction

Practical Performance


Residue number system for Montgomery multiplication:

$$a \mapsto a' = a \cdot r \pmod{n} \quad \text{where} \quad \gcd(r, n) = 1.$$

Montgomery product c' of residues a' and b' defined as

$$c' = a' \cdot b' \cdot r^{-1} \pmod{n}$$

 Practice: Use $r = 2^k$ for fast computation (next slide)



Multiplication (4)

- Overview

- Introduction

- Hardware Design

- Hardware for $GF(2^n)$

- Hardware for $GF(p)$

- Number Representation
- Addition
- Addition (2)
- Addition (3)
- Addition (4)
- Addition (5)
- Subtraction
- Multiplication
- Multiplication (2)
- Multiplication (3)
- Multiplication (4)
- Squaring
- Reduction


- Practical Performance

Binary add-shift algorithm for Montgomery multiplication:

Require: $A' < 2^k, B' < 2^k$, modulus $n, r = 2^k$

Ensure: $U = A' \cdot B' \cdot 2^{-k}$ such that $0 \leq P < 2n$

 - 1: $U := 0$
- 2: **for** $i = 0$ to $k - 1$ **do**
- 3: $U := U + A_i \cdot B$
- 4: **if** U is odd **then**
- 5: **then** $U := U + n$
- 6: **end if**
- 7: $U := U/2$
- 8: **end for**



Squaring

● Overview

Introduction

Hardware Design


Hardware for $GF(2^n)$

Hardware for $GF(p)$

- Number Representation
- Addition
- Addition (2)
- Addition (3)
- Addition (4)
- Addition (5)
- Subtraction
- Multiplication
- Multiplication (2)
- Multiplication (3)
- Multiplication (4)
- Squaring
- Reduction

Practical Performance

 - in $GF(p)$ usually done with multiplication HW
- special HW can make use of special structure
 - ◆ reuse intermediate results
 - ◆ but: increase in area



Reduction

● Overview

Introduction

Hardware Design

Hardware for $GF(2^n)$

Hardware for $GF(p)$

- Number Representation
- Addition
- Addition (2)
- Addition (3)
- Addition (4)
- Addition (5)
- Subtraction
- Multiplication
- Multiplication (2)
- Multiplication (3)
- Multiplication (4)
- Squaring
- Reduction


Practical Performance

Reduction following addition/ subtraction ($c = a \pm b$):

- if $a + b \geq n$, compute $a + b - n$
- if $a - b < 0$ compute $a + n - b$

Reduction following multiplication/ squaring ($c = a^2$ or $c = a \cdot b$):

 - use interleaved or montgomery multiplication (reduction included)
- else: compute remainder of c/n



Timings

● Overview

Introduction

Hardware Design

Hardware for $GF(2^n)$

Hardware for $GF(p)$

Practical Performance

● Timings

● Further Reading

● Literature

Tradeoff time vs. area.

⇒ optimize **area-time (AT)** product

Timings for finite field/ ECC operations of some hardware platforms:

FPGA/ASIC	operation	time	reference
FPGA	512bit multiplication $GF(p)$	$2.37ms$	[BP99]
ASIC	160bit multiplication $GF(p)$	$4.1s$	[STK00]
FPGA	163bit ECC scalarmult. $GF(2^n)$	$144s$	[GCE ⁺ 01]
FPGA	191bit ECC scalarmult. $GF(p)$	$3ms$	[OP01]



Further Reading

- Overview

- Introduction

- Hardware Design

- Hardware for $GF(2^n)$

- Hardware for $GF(p)$


- Practical Performance

- Timings

- Further Reading

- Literature

 - Excellent and brief overview of hardware adders and multipliers for arithmetic in $GF(p)$ given in [Ç. K. Koç96]. Very useful!
- For fields $GF(2^n)$, refer to [SP98]. An overview over different types of multipliers over extensions fields of characteristic two and their optimization is presented.



Literature

● Overview

Introduction

Hardware Design

Hardware for $GF(2^n)$

Hardware for $GF(p)$

Practical Performance

● Timings

● Further Reading

● Literature

References

- [BP99] T. Blum and C. Paar. Montgomery modular multiplication on reconfigurable hardware. In *Proceedings of the 14th IEEE Symposium on Computer Arithmetic (ARITH-14)*, pages 70–77, 1999.
- [Ç. K. Koç96] Ç. K. Koç. RSA Hardware Implementation. RSA Laboratories Technical Report TR-801, RSA Laboratories, Version 1.0 – April 19th, 1996.
- [GCE⁺01] N. Gura, S. Chang, H. Eberle, G. Sumit, V. Gupta, D. Finchelstein, E. Goupy, and D. Stebila. An End-to-End Systems Approach to Elliptic Curve Cryptography. In Ç. K. Koç and C. Paar, editors, *Cryptographic Hardware and Embedded Systems — CHES 2001*, volume LNCS 1965, pages 351–366. Springer-Verlag, 2001.
- [OP00] G. Orlando and C. Paar. A High-Performance Reconfigurable Elliptic Curve Processor for $GF(2^m)$. In Ç. K. Koç and C. Paar, editors, *Cryptographic Hardware and Embedded Systems — CHES 2000*, volume LNCS 1965. Springer-Verlag, 2000.
- [OP01] G. Orlando and C. Paar. A Scalable $GF(p)$ Elliptic Curve Processor Architecture for Programmable Hardware. In Ç. K. Koç, D. Naccache, and C. Paar, editors, *Workshop on Cryptographic Hardware and Embedded Systems — CHES 2001*, volume LNCS 2162, pages 348–363. Springer-Verlag, May 14-16, 2001.
- [SP98] L. Song and K. K. Parhi. Low energy digit-serial/parallel finite field multipliers. *Journal of VLSI Signal Processing*, 19(2):149–166, June 1998.
- [STK00] E. Savas, A. F. Tenca, and Ç. K. Koç. A scalable and unified multiplier architecture for finite fields $gf(p)$ and $gf(2)$. In Ç. K. Koç and C. Paar, editors, *Cryptographic Hardware and Embedded Systems — CHES 2000*, volume LNCS 1965, pages 281–296. Springer-Verlag, 2000.